




WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

Task 2:

Download the Data Sheets of the **SN74ALS163 Synchronous 4-Bit Binary Counter** from Texas Instruments' Web site. Use the available **CAD tools to design, simulate and compile a functionally** equivalent circuit on your **Xilinx Spartan-6 chip**. However, downloading the bit file to your Nexys 3 Board is **NOT** required.

Algorithm of SN74ALS163 Synchronous 4-Bit Binary Counter

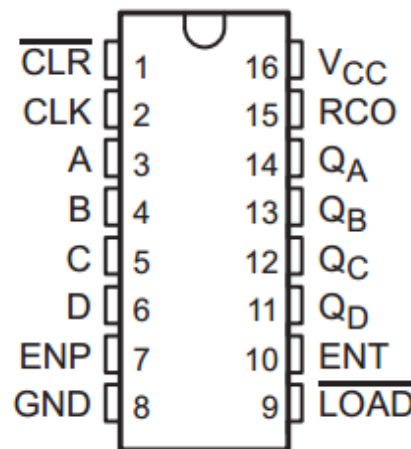The task elaborates the functionally equivalent circuit of SN74ALS163 Synchronous 4-Bit Binary Counter. To execute this task, we have some inputs and outputs. Look the figure below.



SN74ALS163

The counter can be present to any number between 0 and 15. Furthermore, it can start with any number between these numbers. It is possible because we can set up a low level at the load (LOAD). Consequently, the initial count will be the value in the input A, B, C, D. The CLR input when active in low can clear the count to 0000. Also, we have the inputs ENP and ENT that are conditional to count because both must be high to count and ENT is a conditional to enable RCO. RCO, always produces a high-level pulse while the count is 15.

I developed a finite state machine to reproduce the functionally equivalent circuit of SN74ALS163. To test the operation, I created a file .do to test the correct operation.




WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

- I checked the CLR. When it is the low-level, the output must be 0000;
- I checked the LOAD. When the load is in the low-level, the input: A, B, C, and D is copied to the output: Qa, Qb, Qc, and Qd.
- I checked the RCO because it should be high-level when the output is 1111 = "15".
- I checked the inputs: ENP and ENT because the counter just can work when the ENP and ENT if high-level. In case it doesn't happen, the output cannot change.
- Finally, checked the all counter states.

Simulation - Wave

Look the wave below:

 



WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

Counter_vhdl.vhd

```
55         next_state <= s9;
56     elsif (vector = "1010") then -- 10
57         next_state <= s10;
58     elsif (vector = "1011") then -- 11
59         next_state <= s11;
60     elsif (vector = "1100") then -- 12
61         next_state <= s12;
62     elsif (vector = "1101") then -- 13
63         next_state <= s13;
64     elsif (vector = "1110") then -- 14
65         next_state <= s14;
66     elsif (vector = "1111") then -- 15
67         next_state <= s15;
68     end if;
69     else
70         vector_Q <= "0000";
71     end if;
72 when load_in =>
73 when clear =>
74 when s0 =>
75     vector_Q <= "0000";
76     Rco <= '0';
77     if (ENP = '1' and ENT = '1' ) then
78         next_state <= s1;
79     else
80         next_state <= s0;
81     end if;
82 when s1 =>
83     vector_Q <= "0001";
84     Rco <= '0';
85     if (ENP = '1' and ENT = '1') then
86         next_state <= s2;
87     else
88         next_state <= s1;
89     end if;
90 when s2 =>
91     vector_Q <= "0010";
92     Rco <= '0';
93     if (ENP = '1' and ENT = '1') then
94         next_state <= s3;
95     else
96         next_state <= s2;
97     end if;
98 when s3 =>
99     vector_Q <= "0011";
100    Rco <= '0';
101    if (ENP = '1' and ENT = '1') then
102        next_state <= s4;
103    else
104        next_state <= s3;
105    end if;
106 when s4 =>
107     vector_Q <= "0100";
108     Rco <= '0';
109     if (ENP = '1' and ENT = '1') then
```



WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

Counter_vhdl.vhd

```
110         next_state <= s5;
111     else
112         next_state <= s4;
113     end if;
114     when s5 =>
115         vector_Q <= "0101";
116         Rco <= '0';
117         if (ENP = '1' and ENT = '1') then
118             next_state <= s6;
119         else
120             next_state <= s5;
121         end if;
122     when s6 =>
123         vector_Q <= "0110";
124         Rco <= '0';
125         if (ENP = '1' and ENT = '1') then
126             next_state <= s7;
127         else
128             next_state <= s6;
129         end if;
130     when s7 =>
131         vector_Q <= "0111";
132         Rco <= '0';
133         if (ENP = '1' and ENT = '1') then
134             next_state <= s8;
135         else
136             next_state <= s7;
137         end if;
138     when s8 =>
139         vector_Q <= "1000";
140         Rco <= '0';
141         if (ENP = '1' and ENT = '1') then
142             next_state <= s9;
143         else
144             next_state <= s8;
145         end if;
146     when s9 =>
147         vector_Q <= "1001";
148         Rco <= '0';
149         if (ENP = '1' and ENT = '1') then
150             next_state <= s10;
151         else
152             next_state <= s9;
153         end if;
154     when s10 =>
155         vector_Q <= "1010";
156         Rco <= '0';
157         if (ENP = '1' and ENT = '1') then
158             next_state <= s11;
159         else
160             next_state <= s10;
161         end if;
162     when s11 =>
163         vector_Q <= "1011";
164         Rco <= '0';
```



WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

Counter_vhdl.vhd

```
165         if (ENP = '1' and ENT = '1') then
166             next_state <= s12;
167         else
168             next_state <= s11;
169         end if;
170     when s12 =>
171         vector_Q <= "1100";
172         Rco <= '0';
173         if (ENP = '1' and ENT = '1') then
174             next_state <= s13;
175         else
176             next_state <= s12;
177         end if;
178     when s13 =>
179         vector_Q <= "1101";
180         Rco <= '0';
181         if (ENP = '1' and ENT = '1') then
182             next_state <= s14;
183         else
184             next_state <= s13;
185         end if;
186     when s14 =>
187         vector_Q <= "1110";
188         Rco <= '0';
189         if (ENP = '1' and ENT = '1') then
190             next_state <= s15;
191         else
192             next_state <= s14;
193         end if;
194     when s15 =>
195         vector_Q <= "1111";
196         Rco <= '1';
197         if (ENP = '1' and ENT = '1') then
198             next_state <= s0;
199         else
200             next_state <= s15;
201         end if;
202     end case;
203 end process count_process;
204
205 Q_process: process(vector_Q)
206 begin
207     Qa <= vector_Q(0);
208     Qb <= vector_Q(1);
209     Qc <= vector_Q(2);
210     Qd <= vector_Q(3);
211 end process Q_process;
212
213 clk_process: process(CLK)
214 begin
215     --wait until (CLK'event and CLK = '1'); --wait until the rising edge
216     if (CLK'event and CLK = '1') then
217         if (CLR = '0') then
218             present_state <= start;
219         else
```



WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

Counter_vhdl.vhd

```
220         present_state <= next_state;
221     end if;
222 end if;
223 end process clk_process;
224
225 end Behavioral;
226
227
```

Simulation: File .do

```
##### force B 1
#      Macro for the SN7ALS163      # force C 0
##### force D 0
restart # Clear test
# Generates de clock with T = 20ns run 7ns
force CLK 0 0, 1 10ns -r 20ns force CLR 0
run 15ns
# Initial Information force CLR 1
force A 0
force B 0 # Load of the initial condition
force C 0 run 10ns
force D 0 force load 0
force ENP 0 run 10ns
force ENT 0 force load 1
force load 1 # Test of the inputs ENP and ENT
force CLR 1 run 10ns
# Initial condition for A, B, C, D force ENP 1
run 10ns run 15ns
force A 1 force ENT 1
```



WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

Maintain the count

run 15ns

run 150ns

force ENP 1

Test the Inhibit

run 170ns

force ENP 0

File .ucf

PlanAhead Generated physical constraints

NET "A" LOC = T10;

PlanAhead Generated IO constraints

NET "A" IOSTANDARD = LVCMOS33;

PlanAhead Generated physical constraints

NET "B" LOC = T9;

PlanAhead Generated IO constraints

NET "B" IOSTANDARD = LVCMOS33;

PlanAhead Generated physical constraints

NET "C" LOC = V9;

PlanAhead Generated IO constraints

NET "C" IOSTANDARD = LVCMOS33;
NET "CLK" IOSTANDARD = LVCMOS33;

PlanAhead Generated physical constraints

NET "CLR" LOC = M8;
NET "D" LOC = N8;
NET "ENP" LOC = U8;
NET "ENT" LOC = V8;



WESTERN MICHIGAN UNIVERSITY
ECE 5510 APPLICATION SPECIFIC INTEGRATED CIRCUIT DESIGN
Homework Assignment #2

NET "load" LOC = T5;

PlanAhead Generated IO constraints

NET "load" IOSTANDARD = LVCMOS33;
NET "ENP" IOSTANDARD = LVCMOS33;
NET "ENT" IOSTANDARD = LVCMOS33;
NET "D" IOSTANDARD = LVCMOS33;
NET "CLR" IOSTANDARD = LVCMOS33;

PlanAhead Generated physical constraints

NET "Qa" LOC = U16;
NET "Qb" LOC = V16;

PlanAhead Generated IO constraints

NET "Qa" IOSTANDARD = LVCMOS33;
NET "Qb" IOSTANDARD = LVCMOS33;
NET "Qc" IOSTANDARD = LVCMOS33;
NET "Qd" IOSTANDARD = LVCMOS33;
NET "Rco" IOSTANDARD = LVCMOS33;

PlanAhead Generated physical constraints

NET "Qc" LOC = U15;
NET "Qd" LOC = V15;
NET "Rco" LOC = M11;
NET "CLK" LOC = C9;